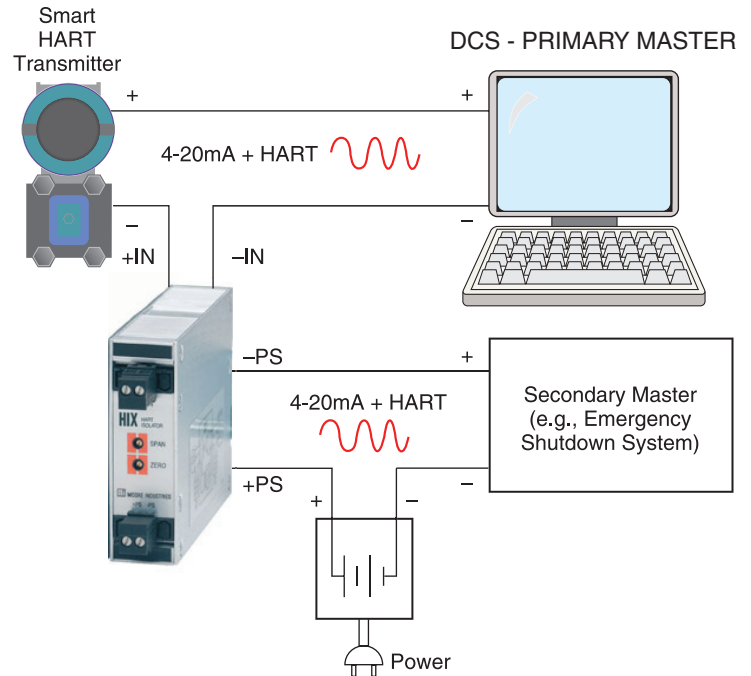


Smart HART Transmitters, Monitors and Interfaces

Additional HART Loops to Share Process Signals

Problem: How can I provide an additional HART output loop to share process signals between existing systems?

Solution: Use the HIT and HIX HART Isolators. They are single input/single output isolators that pass the digital component of the HART signal from the input to the output. The input can be connected in series with the original HART loop before the isolated output is connected to an alternate receiver.



Model Number Example
HIX / 4-20mA / 4-20mA / 12-42DC [DIN]

[Go to Smart HART Transmitters, Monitors and Interfaces Selection Guide](#)