

### Put an End to “Bucking” Power Supplies

**Problem:** We have several loops where we need to use 4-wire transmitters connected to a DCS. However, the DCS is powering its input loops, causing a conflict with the powered transmitters.



**Solution:** Installing an ECT will quickly put an end to your “bucking” power supplies. The ECT operates with powered inputs from both sides, restoring normal loop operations.

#### Model Number Example

**ECT / 4-20MA / 4-20MA / 12-42DC [DIN]**

[Go to Signal Transmitters, Isolators and Converters Selection Guide](#)
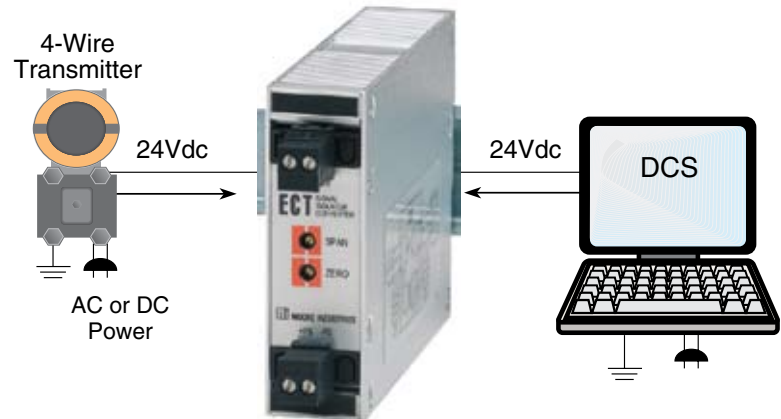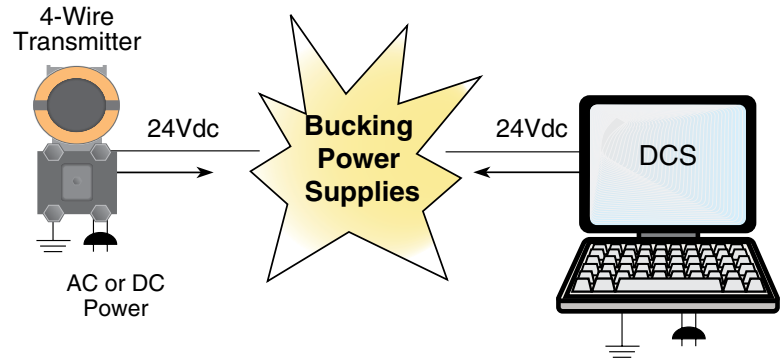
### Signal Transmitters, Isolators and Converters



The ECT Signal Transmitter stops “bucking” power supplies